


E/20/449

Mjewardhana A.R.S.S.

16 bit I/O port

ISA data bus - 8 bits.


16 bit port needs 2 addresses

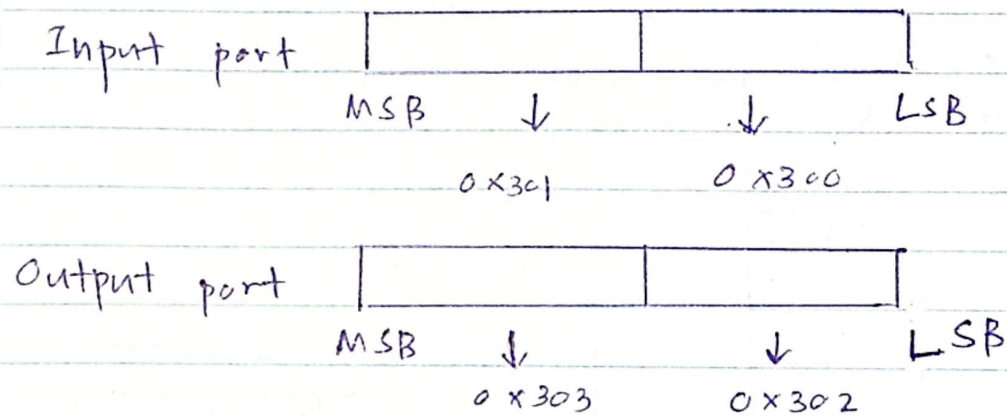






$\therefore$ need to decode 4 addresses total

Address	Binary $A_{15}A_6$	A_1	A_0
$0x300$	0000 0011 0000	00	00
$0x301$	0000 0011 0000	00	01
$0x302$	0000 0011 0000	00	10
$0x303$	0000 0011 0000	00	11

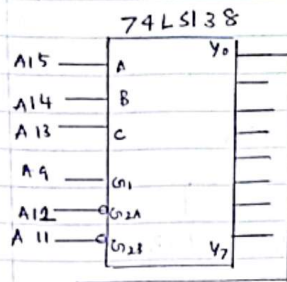$\underbrace{A_{15} : A_2}_{\text{Fixed}}$ $\downarrow$ varies



Address
decoder

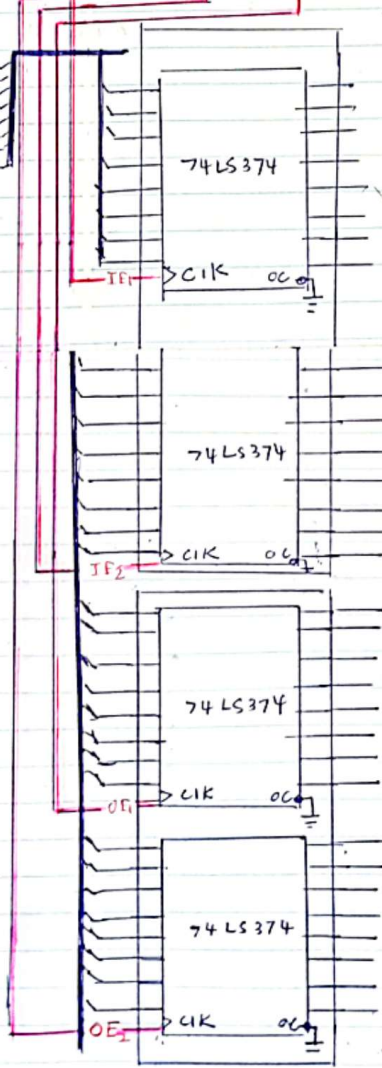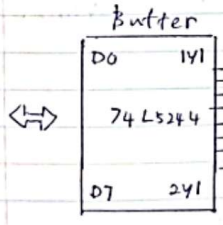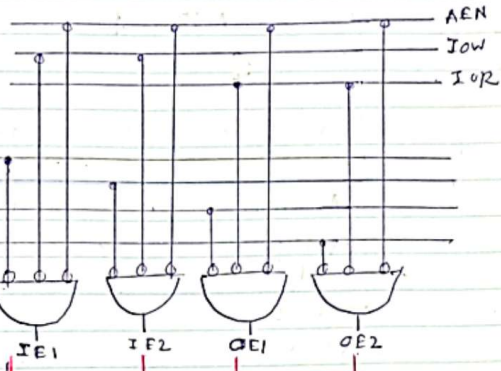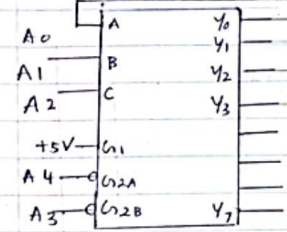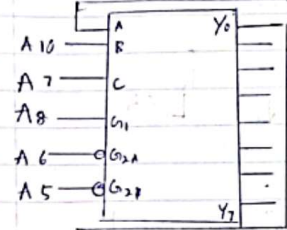

← in

⇒ out